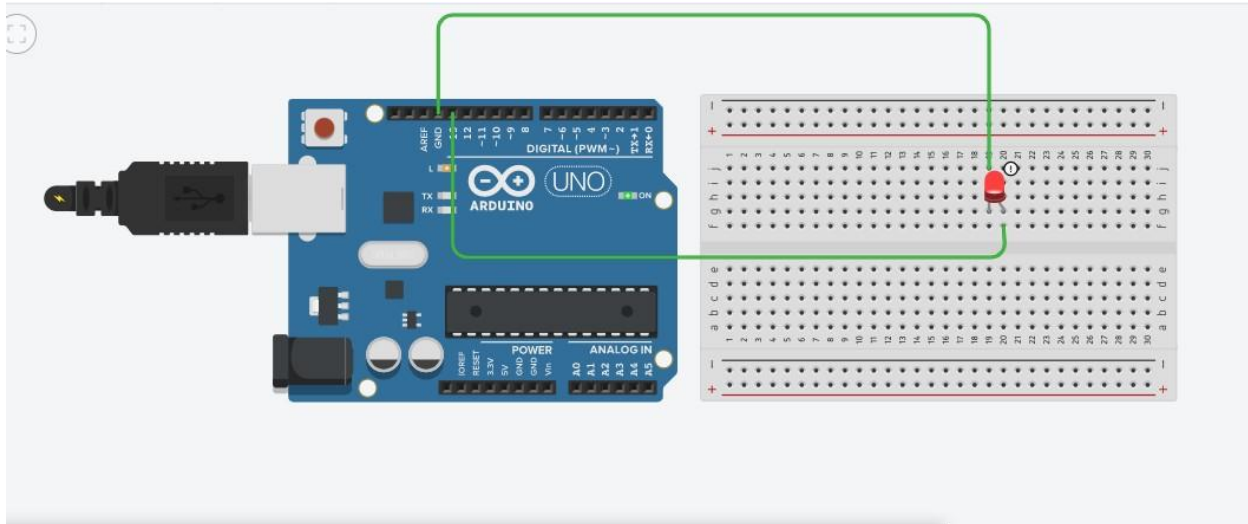


## Experiment 2

### DESIGN AN LED FLASHER

Circuit Diagram:



## Theory:

### CONCEPT USED:

- By using kirchoff's voltage law  
&
- By using kirchoff's current law

### LEARNING AND OBSERVATIONS:

- Connections in Breadboard and wiring.
- How to control arduino and its coding.
- Use of multimeter for continuity.

## **OBSERVATION:**

- Blinking of an LED.
- Relation between software and hardware.

## **PROBLEMS & TROUBLESHOOTING:**

- To select the right port and type of arduino
- To check the loose connections
- To check the connections according to the codes
- To check the continuity of the circuit
- To check the flow of current in the circuit

## **PRECAUTIONS:**

- Handle tools carefully
- Wear gloves
- Do not connect arduino till the circuit is complete

## **OUTCOMES:**

- On and off of an LED
- Used in project works

**Created By-**

Name: RISHABH GUPTA  
ROLLNO: 19BCS3792  
Dept: CSE(BD1 GP.B)  
University: CHANDIGARH UNIVERSITY

